

Solution Key

Exam Sheet



Faculty: Engineering and Design	Department: Renewable Energy Engineering
Academic Year: 2024/2025	Semester: 2 nd Semester
Course Name and Number: Circuits I - 952501	
Instructor Name: A.J.	Coordinator Name:
Midterm Exam <input checked="" type="checkbox"/>	Final Exam
Exam Date: 29/4/2025	Exam Time: 15:00-16:00
Exam Room Number: B203	
Student Name:	Student ID:

Problem No.	CLO	Full Points	Student's Point
Problem (0)+(1)	CLO (1)	15 Points	
Problem (2)+(3)	CLO (1)	12 Points	
Total		25 Points + 2 BONUS	

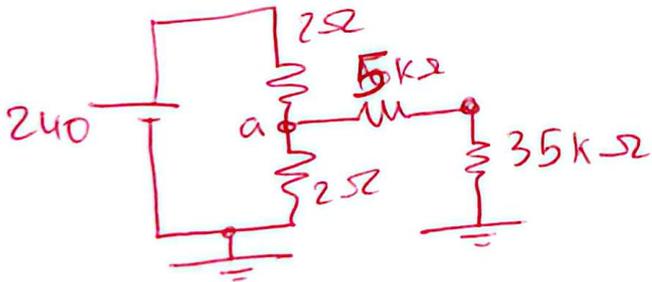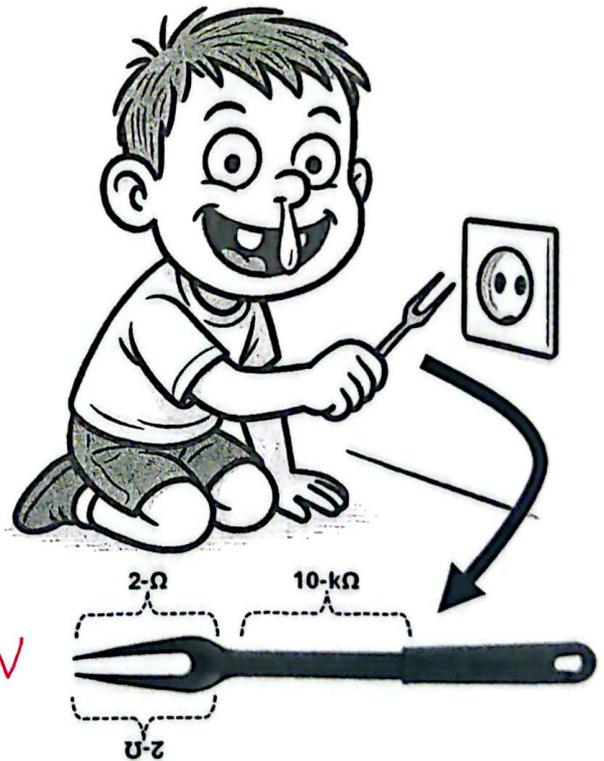Problem 0 (CLO1)

6 Points

A naughty child is pushing a 2-throng fork (شوكة بحريتين) in a DC electrical socket with a voltage of 240V. One terminal of the socket is connected to earth and the other is +240V. The child is also sitting on earth. His resistance from hand to foot is 35-kΩ. The resistance of every throng (حرية) of the fork is 2-Ω. The fork's handle (مقبض الشوكة) is made of wood and a resistance of 5-kΩ. What current will run through the child? How much power will be consumed in the fork? DRAW the equivalent circuit first.



$$V_a = 240 \cdot \frac{2 // 40k}{2 + 2 // 40k} = 119.997 \text{ V}$$

$$I_{child} = \frac{V_a}{40k} = \frac{119.997}{40k} = 2.999925 \text{ mA} \approx 3 \text{ mA}$$

$$P_{fork} = P_{thru1} + P_{thru2} + P_{handle}$$

$$P_{thru1} = \frac{V_{thru1}^2}{2} = \frac{(120.003)^2}{2} = 7200.36 \text{ W}$$

$$P_{thru2} = \frac{V_{thru2}^2}{2} = \frac{119.997^2}{2} = 7199.64 \text{ W}$$

$$P_{handle} = I_{child}^2 \cdot R_{handle} = (2.999925 \text{ mA})^2 \cdot 5k = 44.99775 \text{ mW} \approx 45 \text{ mW}$$


$I_{child} = 2.999925 \text{ mA}$	$P_{fork} = 14,400.045 \text{ W}$
-----------------------------------	-----------------------------------

$$P_{fork} = 14,400.045 \text{ W}$$

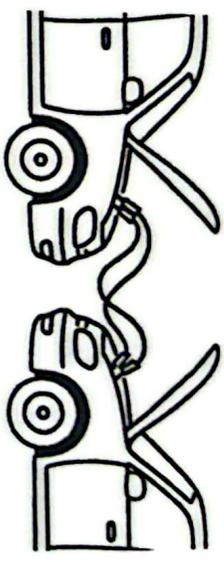
Problem 1 (C101)

9 Points

The car on the left is charging the battery of the car on the right. The car on the left has a battery with a voltage of 12-V. The one on the right has a battery that only has 6-V. The charging is happening using two cables as shown. Each cable has a resistance of 0.5-Ω. During charging the car on the left has its lights on. The lights are connected to the battery and have a resistance of 1-Ω. The car on the right also has its lights on and they have a resistance of 2-Ω.




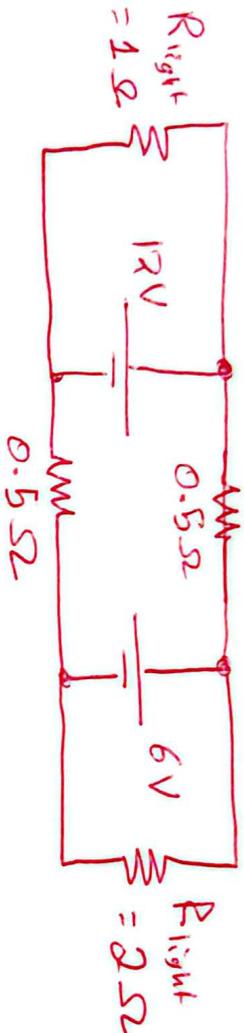a) Draw the equivalent circuit of this problem.



b) Find the power absorbed the 6-V battery of the car on the right.

Using superposition:

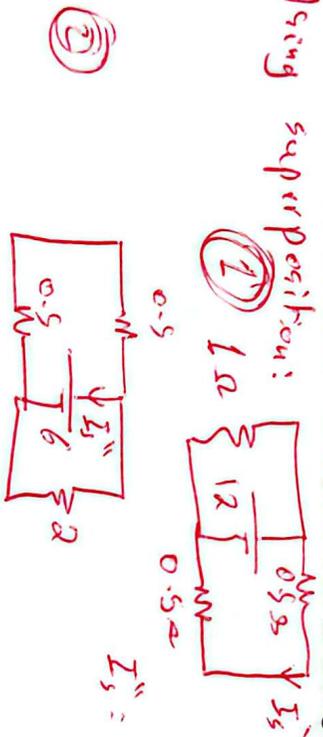

$$I_s' = \frac{12}{0.5 + 0.5} = 12A$$

$$I_s'' = -\left(\frac{6}{2} + \frac{6}{0.5+0.5}\right) = -(3+6) = -9A$$


$$I_s = I_s' + I_s'' = 12 - 9 = 3A$$

$$P_{6V} = 6 \times 3 = 18W_{att}$$

$$P_{6V} = 18W_{att}$$

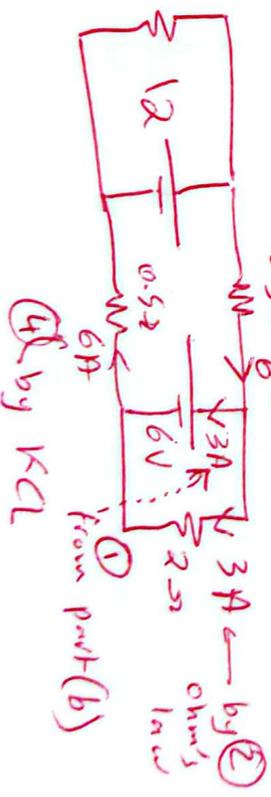c) Find the power lost in the charging cables (the two cables together).

$$P_{cables} = 6^2 \times 0.5 + 6^2 \times 0.5 = 36W_{att}$$



$$P_{cables} = 36W_{att}$$

Problem 2 (C101)

6 Points

You have 10 bulbs, each rated at 100V, 5 Watts. (i.e. When the bulb is connected to a 100 V DC source, it consumes 5 Watts). The bulb behaves like an ideal resistor. Answer the following:


a) If all 10 bulbs are connected in series, and are fed together from a single 100-V source, what is the total power they will consume in Watts?

$$R_{bulb} = \frac{V^2}{P} = \frac{(100)^2}{5} = 2000 \Omega$$

For 10 bulbs in series: $R_{Total} = 10 \times 2000 = 20k \Omega$

$$P_{Total} = \frac{V^2}{R_{Total}} = \frac{(100)^2}{20k} = 0.5 W$$

Series = 500 mW

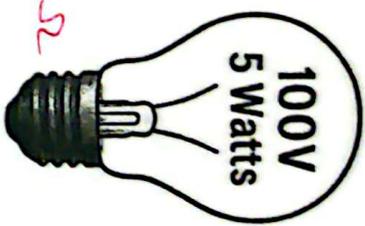


b) If all 10 bulbs are connected in parallel, and are fed together from a 100-V source, what is the total power they will consume in Watts?

$$P_{Total} = 5 \times 10 = 50 W$$

Parallel = 50W

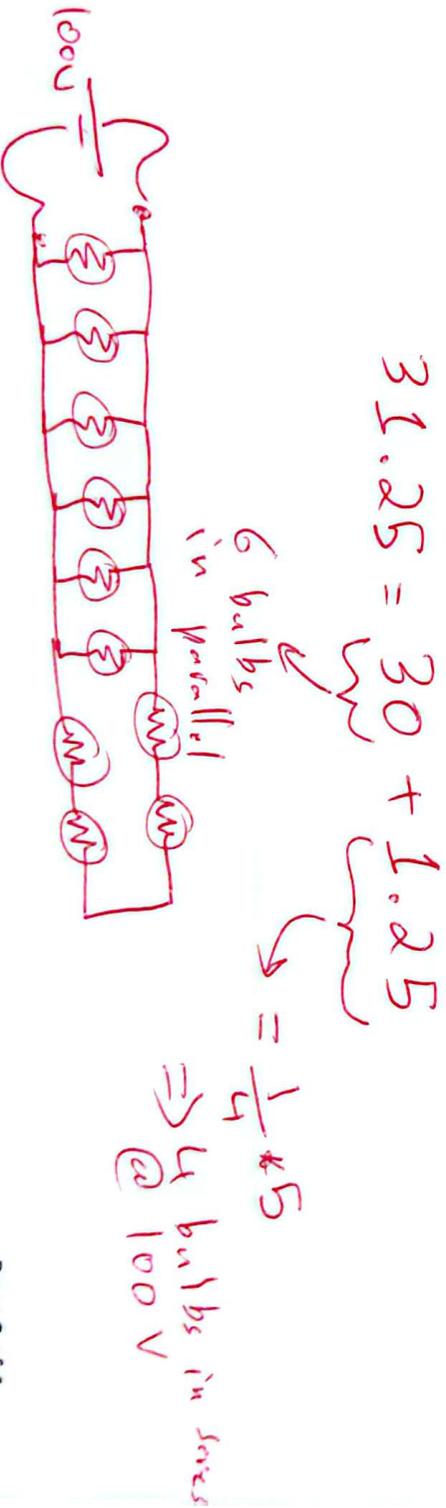c) Draw a possible connection of the ten bulbs that would consume a total of 31.25 Watts when fed from a single 100V DC source.




Problem 3 (CLO1)

6 Points

The circuit you see on the right is called a voltage divider. It is used to reduce the voltage of a high voltage source in order to feed a load that needs a lower voltage. The source here is 24-V. The load, R_L , will be connected between nodes (a) and (b) (in parallel with the 200- Ω resistor). Plot the following graphs as functions of the load resistance R_L :

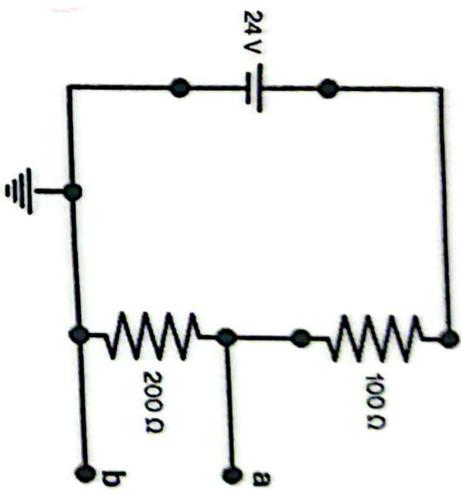- Load voltage V_L versus R_L
- Source current I_S versus R_L
- Power dissipated in the 100- Ω resistor (P_{100}) versus R_L



Clearly mark any important values on the x- and y-axes. Make sure the graphs clearly show the limiting behavior as R_L approaches infinity.

$$24 \times \frac{200 // \infty}{100 + 200 // \infty} = 16$$

