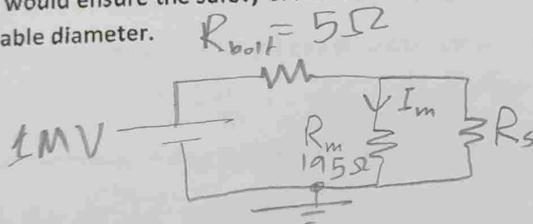


Solution Key

Faculty: Engineering	Department: Renewable Energy Engineering
Academic Year: 2024/2025	Semester: 1 st Semester
Course Name and Number: Electrical Circuits I (0952501)	
Instructor Name: A. Jayyousi	Midterm Exam <input checked="" type="checkbox"/>
Exam Date: 4/12/2024	Exam Time: 12:00-13:00
Student Name:	ID Number:
8 Points	

Problem 1 (CLO1)

A minaret has a height of 30-meters from ground to its highest point. The minaret has a total electric resistance of $195\text{-}\Omega$ (from tip to earth). To protect the minaret from thunderbolts (صواعق), a lightning suppressor system (مانع صواعق) is installed. The system is a simple copper cable ($\sigma = 5.8 \times 10^6 \text{ S/m}$) extending from the highest point of the minaret to ground. The cable has approximately the same length as the height of the building. The minaret can withstand (تحتمل) a maximum of 2000A when hit by thunderbolts. If the thunderbolt causes a higher current through the minaret, it will catch fire, explode or get heavily damaged. The thunderbolt itself has a resistance of $5\text{-}\Omega$. The cloud can be modelled as a DC voltage source between earth & sky with a voltage of 1 Million Volt. Find the maximum resistance of the lightning suppressor cable that would ensure the safety of Allah's house. Then find the minimum required cable diameter.



$$I_{\text{minaret, max}} = 2000 \text{ A}$$

$$V_{\text{minaret, max}} = R_{\text{minaret}} \cdot I_{\text{minaret, max}} = 195 \cdot 2000$$

$$V_{\text{minaret, max}} = 390,000 \text{ V}$$

$$R_{\text{total}} = R_{\text{minaret}} \parallel R_{\text{suppress}}$$

Voltage Division Rule:

$$V_{R_{\text{total}}} = 1\text{M} \cdot \frac{R_{\text{total}}}{5 + R_{\text{total}}} = 390\text{k}$$


$$R_{\text{total}} = 0.39 \cdot 5 + 0.39 \cdot R_{\text{total}}$$

$$0.61 R_{\text{total}} = 1.95 \Rightarrow R_{\text{total}} \approx 3.1967 \Omega$$

$$R_{\text{suppress}} = 3.25 \Omega$$

$$D_{\text{cable}} = 1.423 \text{ mm}$$

Lightning Suppressor cable

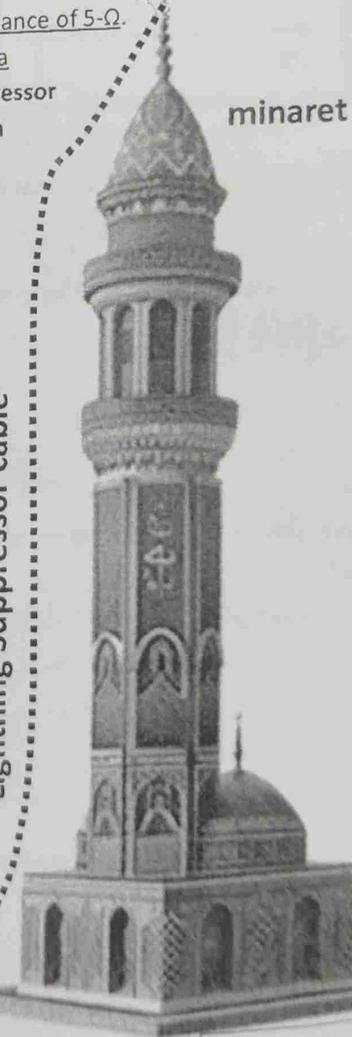

F134-D1 (ABET) Rev. a

Ref.: Deans' Council Session (21/2022-2023) Decision No.: D1

Date: 05/02/2023

Page 1 of 4

$$R_{\text{minaret}} \parallel R_{\text{sup}} = 3.1967$$

$$R_{\text{minaret}} = R_{\text{sup}}$$

$$195 R_{\text{sup}} = 3.1967 \cdot 195 + 3.1967 \cdot R_{\text{sup}}$$

$$R_{\text{sup}} \approx 3.25 \Omega$$

$$R = \frac{L}{\sigma A} = \frac{30}{5.8 \times 10^6 \cdot \frac{\pi D^2}{4}} = 3.25$$

$$D = \sqrt{\frac{120}{5.8 \times 10^6 \cdot \pi \cdot 3.25}}$$

$$D = 1.423 \text{ mm}$$

Problem 2 (CLO1)

4 Points


Look at the 6 resistors shown on the right. The resistors are identical. Each one has a value of 3-Ω and a maximum power rating of 12-Watts. Find the following:

$$a) R_{ad} = \left(3 // (3+3) \right) + \left(3 // (3+3) \right) \\ = 4$$

$$R_{ad} = 4 \Omega$$

b) R_{ab}

$$R_{ab} = 2 \Omega$$

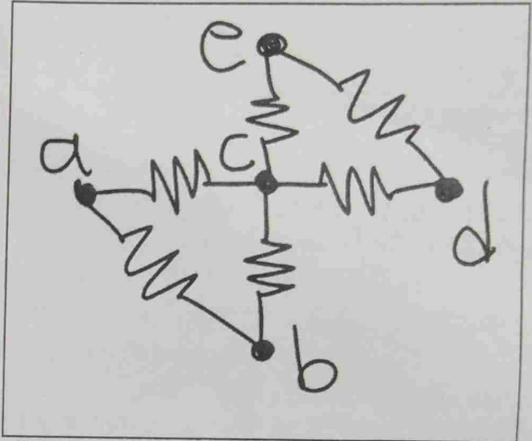

c) What is the maximum voltage that can be applied across terminals (a) and (d) without damaging the resistors?

$$\frac{(V_{max})^2}{3} = 12 \Rightarrow V_{max} = \sqrt{12 \times 3} = 6V$$

$$V_{ac, max} + V_{cd, max} = 6 + 6 = 12 = V_{ad, max}$$

$$V_{ad, max} = 12V$$

d) If the resistor connecting points (c) and (b) is burnt and becomes an open-circuit, what is the new value of R_{ad} then?



$$R_{ac} + R_{cd} // (R_{ce} + R_{ed}) = 3 + 3 // 6 = 3 + 2 = 5$$

$$R_{ad} = 5 \Omega$$

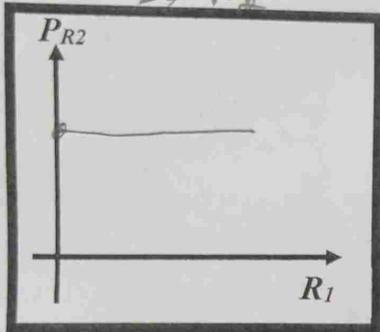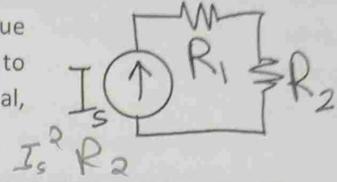
Problem 3 (CLO1)

3 Points


An independent current source, I_s , is connected in series with two resistors, R_1 and R_2 . Draw a rough plot of the power consumed by resistor R_2 versus the following: the value of R_1 , the value of I_s , and the value of R_2 . No exact values are required, but you need to show the correct form of the plot (linear rising, linear falling, quadratic, exponential, etc..). Also, the graph should show P_{R2} when the x-axis variable is zero.



(I_s and R_2 constant)

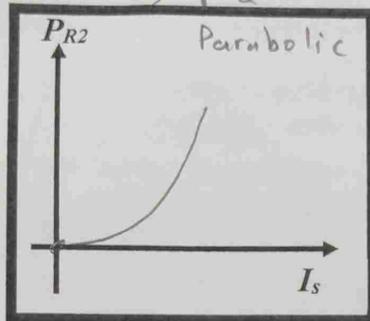

(R_1 and R_2 constant)

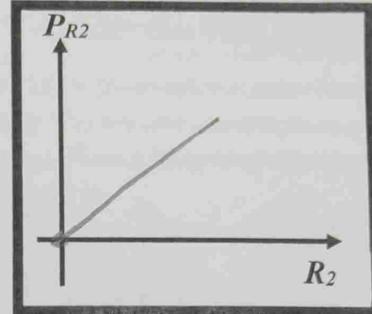

(I_s and R_1 constant)

Problem 4 (CLO1)

6 Points

A bulb consumes 60 Watts to produce a certain amount of light when operated from 240VDC.

- a) What operating voltage is needed to make the bulb give half the amount of light?

$$P = 30 \text{ Watts}$$

$$\frac{V^2}{R} = 30$$


$$V = \sqrt{30 \cdot R} = \sqrt{30 \cdot 960} \approx 169.7 \text{ V}$$

$$\frac{240^2}{R} = 60 \Rightarrow R = 960 \Omega$$

$$V = 169.7 \text{ V}$$

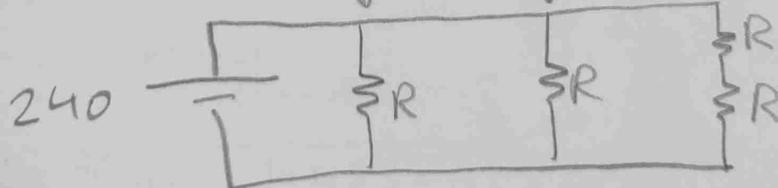- b) If you have an infinite quantity of this type of bulb, what combination of bulbs should you use to achieve a total power consumption of 150-Watts when operating from a 240-V source? Draw the combination.


$$150 \text{ W} = 60 \text{ W} + 60 \text{ W} + 30 \text{ W}$$



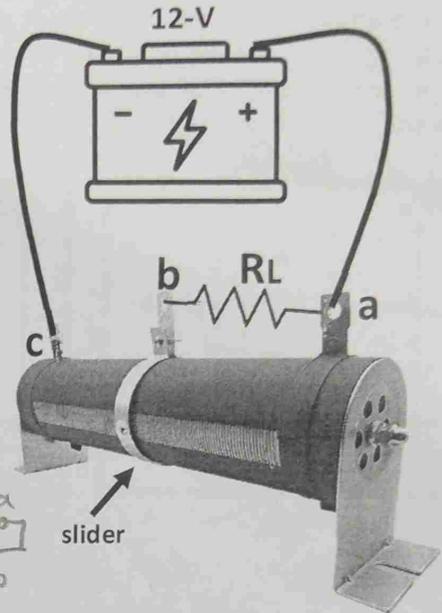Problem 5 (CLO1)

6 Points

The image on the right shows a potentiometer (a variable resistor). The potentiometer has three terminals: a, b & c. The full resistance of this potentiometer is $R_{ac}=1k\Omega$. The ring-shaped slider is connected to terminal (b) and provides a variable resistance (R_{ab} & R_{bc}). A load, R_L , can be connected between terminals (a) and (b), while a 12-V battery is connected between terminals (a) and (c). Assuming the slider is placed exactly in the middle of the potentiometer, find the following:



- a) Range of voltage which any load (R_L) could experience (loads assumed to extend from zero resistance to infinity). Give your answer in the form of $[V_{\text{minimum}}, V_{\text{maximum}}]$.


Range is limited by $R_L=0$ and $R_L=\infty$
when $R_L=0 \Rightarrow V_{ab}=0$

When $R_L=\infty \Rightarrow V_{ab}=6V$

$[V_{\text{min}}, V_{\text{max}}] = [0, 6]$

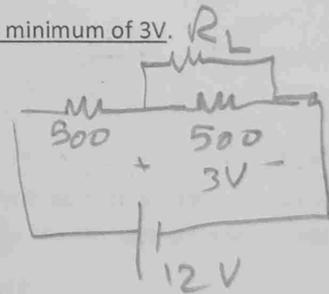- b) What is the minimum load resistance, R_L , that would ensure the load gets a minimum of 3V.

$$3 = 12 \cdot \frac{R_L // 500}{500 + R_L // 500}$$



$$1500 + 3R_T = 12R_T$$

$$R_T = \frac{1500}{9} = 166.\bar{6}$$

$R_L = 250 \Omega$

$$\frac{500R_L}{500+R_L} = 166.\bar{6}$$

$$500R_L = 83,333.\bar{3} + 166.\bar{6}R_L \Rightarrow R_L = \frac{83,333.\bar{3}}{333.\bar{3}} = 250 \Omega$$